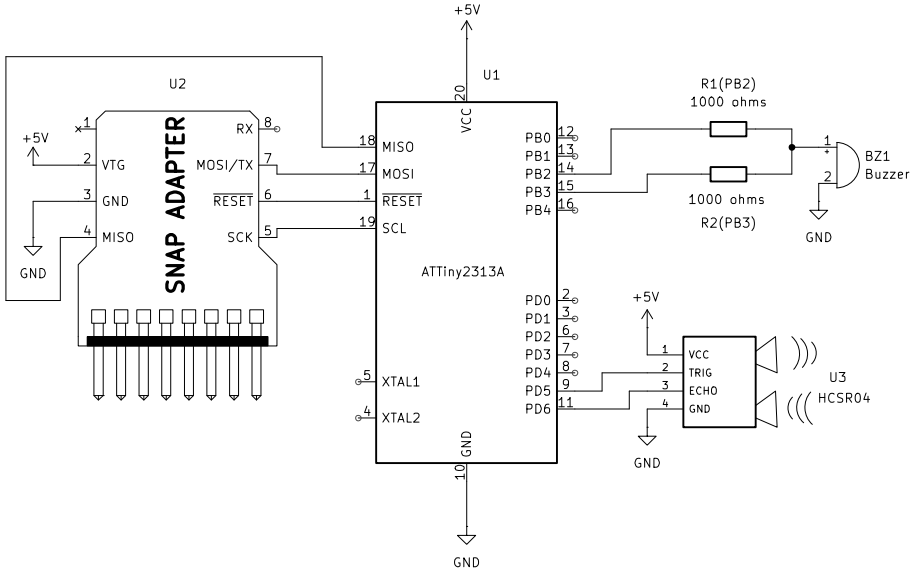Lab 2 Circuit by Komaldeep Taggar & Antony Feng